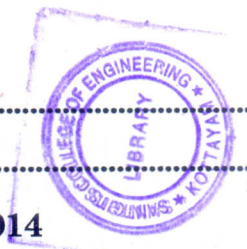


F 3128

(Pages : 4)

Reg. No.....

Name.....



**B.TECH. DEGREE EXAMINATION, NOVEMBER 2014**

**Third Semester**

Branch : Applied Electronics and Instrumentation/Electronics and Communication/  
Electronics and Instrumentation/Instrumentation and Control Engineering

AI 010 303/EC 010 303/EI 010 303/IC 010 303—NETWORK THEORY [AI, EC, EI, IC]

(New Scheme—2010 Admission onwards)

[Regular/Improvement/Supplementary]

Time : Three Hours

Maximum : 100 Marks

*Assume any missing data suitably.*

**Part A**

*Answer all questions briefly.  
Each question carries 3 marks.*

1. State Superposition theorem as applied to d.c. circuits.
2. Obtain impulse response of a series RL circuit.
3. Write the steps in nodal analysis of solving an electrical network.
4. Find the Laplace Transform of  $e^{at}$ .
5. Define the transmission parameters of a two-port network.

(5 × 3 = 15 marks)

**Part B**

*Answer all questions.  
Each question carries 5 marks.*

6. Use source transformation to calculate the current I in the network ? Fig. 1


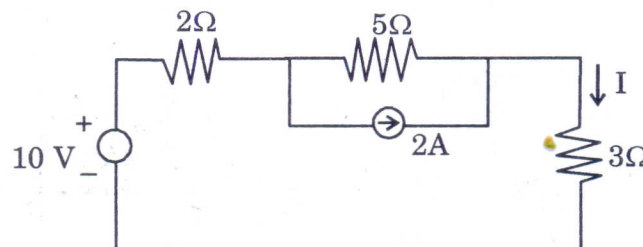


Fig. 1

Turn over

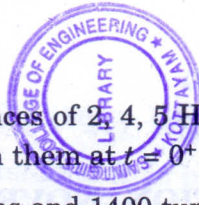

- 7. Initially relaxed inductances of 2, 4, 5 Henries are connected in parallel across a 12 A source at  $t = 0$ . Find the currents in them at  $t = 0^+$ .
- 8. Two coils having 800 turns and 1400 turns respectively are placed close to each other such that, 60 % of the flux produced by one coil links the other. If a current of 10A flowing in the first coil produces a flux of 0.5 mWb, find the inductance of the second coil.
- 9. Find the inverse Laplace Transforms of :


$$\frac{s^2 + 3}{(s^2 + 2s + 5)(s + 2)}$$

- 10. Explain the condition for symmetry for two-port network. Show the symmetry for z-parameters. (5 × 5 = 25 marks)

**Part C**

Answer all questions.  
Each full question carries 12 marks.


- 11. Find "i" in the circuit shown in Fig. 2 using Superposition theorem :

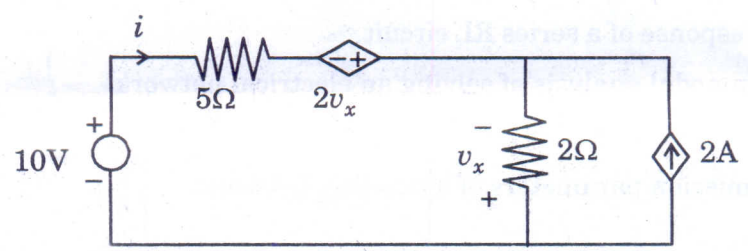

**Fig. 2**

Or

- 12. What is the value of R such that maximum power transfer takes place from the sources to R in the circuit shown in Fig. 3 ? Determine the amount of the maximum power :

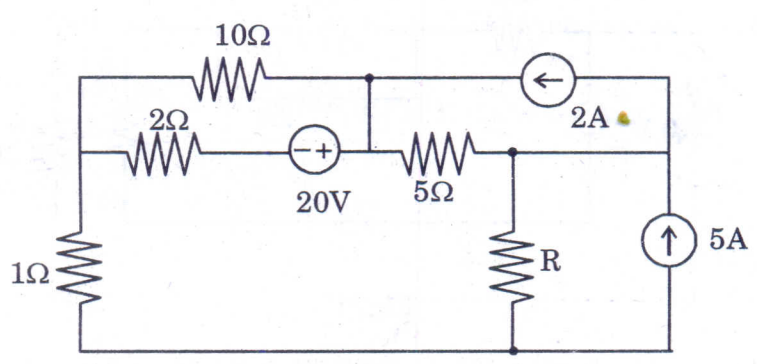

**Fig. 3**

13. At time  $t = 0$ , the switch K is opened for the network shown in Fig. 4. Find  $V_1(t)$  and  $V_2(t)$  for  $t \geq 0$ .

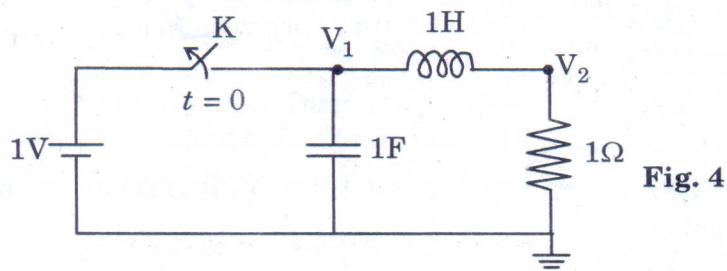


Fig. 4

Or

14. A series RLC circuit with zero initial conditions is connected to 110 V d.c. source at  $t = 0$ . If  $L = 1\text{H}$ ,  $C = \frac{1}{16}\text{F}$  and R is (a)  $4\ \Omega$  ; (b)  $8\ \Omega$ , find  $i(t)$  in the circuit in both cases and plot it.

(6 + 6 = 12 marks)

15. Find the Thevenin and Norton equivalent circuits for the network shown in Fig. 5.

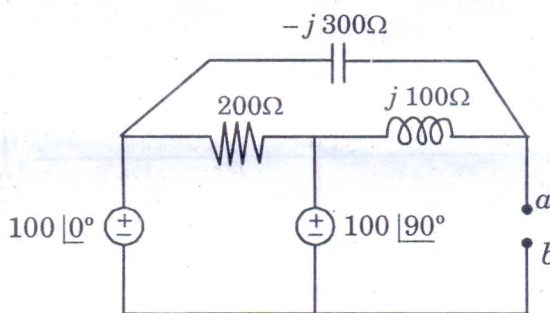


Fig. 5

Or

16. Calculate the current  $I_x$  using (a) nodal analysis ; and (b) mesh analysis and verify the result for the network in Fig. 6.

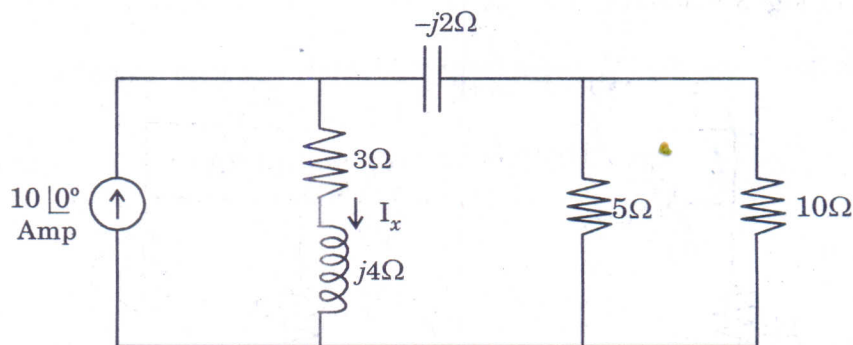


Fig. 6

Turn over

17. A series RLC circuit, with  $R = 180 \Omega$ ,  $L = 0.5 \text{ H}$  and  $C = 100 \mu\text{F}$ , has a sinusoidal voltage source  $v = 500 \sin(500t + \phi)$  volts. Find from basics, using Laplace Transform, an expression for the resulting current, if the switch is closed at a time corresponding to  $\phi = 45^\circ$ . Find the value of current 0.05 second after switching on.

Or

18. A series circuit has  $R = 0.5 \Omega$  and  $L = 0.2 \text{ H}$  and  $C = 2\text{F}$ . It is connected to a constant voltage variable frequency supply :
- Find the driving point admittance and plot its poles and zeros.
  - Using the pole-zero plot, find expressions for amplitude response and phase response.
  - Find magnitude and phase of admittance function at  $\omega = 1$ .
19. (a) Determine the hybrid parameters of the network shown in Fig. 7 below :

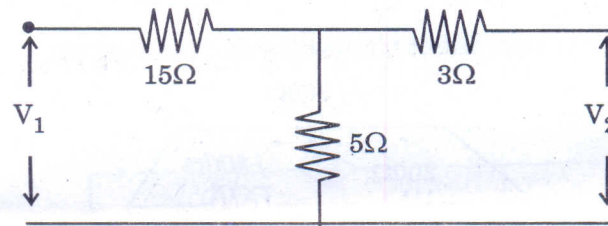


Fig. 7

(6 marks)

- (b) Two 2-port networks,  $N_1$  and  $N_2$  are interconnected such that their input ports are in series and the output ports are in parallel. If  $H_1$  and  $H_2$  are the hybrid parameter matrices of  $N_1$  and  $N_2$  respectively, show from basis that the hybrid parameter matrix of the interconnection is  $H = H_1 + H_2$ .

Or

20. A certain network has a specified transfer function. Obtain the expressions for  $a(\omega)$  and  $\theta(\omega)$

given that  $H(s) = \frac{(s+20)}{5(s+4)}$ . Then find the steady state output  $y(t)$  when the input is

$$x(t) = \cos 2t + \cos 10t + \cos 50t.$$

(5 × 12 = 60 marks)