

Register No.: Name:

SAINTGITS COLLEGE OF ENGINEERING (AUTONOMOUS)

(AFFILIATED TO APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY, THIRUVANANTHAPURAM)

FIFTH SEMESTER B.TECH DEGREE EXAMINATION (Regular), DECEMBER 2022 ELECTRONICS AND COMMUNICATION ENGINEERING (2020 SCHEME)

Course Code : 20ECT301

Course Name: Linear Integrated Circuits

Max. Marks : 100

Duration: 3 Hours

PART A

(Answer all questions. Each question carries 3 marks)

1. A differential amplifier has common mode gain $A_c=0.1$ and difference mode gain $A_d=200$. Let the input signals be $V_1=1050\mu V$ and $V_2=950\mu V$. Calculate the output voltage and CMRR.
2. Define slew rate and explain its effect at the output of an Op-Amp.
3. Design a non-inverting amplifier with gain 11.
4. Distinguish between virtual ground and actual ground.
5. Sketch the circuit of a monostable multivibrator using Op-Amp.
6. Design a first order Butterworth low pass filter with $f_L = 1\text{KHz}$ and pass band gain of 3.
7. Draw the functional diagram of 555 Timer IC.
8. Explain the necessity of using low pass filter in a PLL.
9. Define line regulation and load regulation.
10. List the specifications of D/A converter.

PART B

(Answer one full question from each module, each question carries 14 marks)

MODULE I

11. a) Derive the expression for differential mode gain, common mode gain and CMRR of a dual input balanced output differential amplifier. (10)
- b) Explain the working of Widlar current source. (4)

OR

12. a) Explain the block diagram of an Op-Amp. (6)
- b) Explain i) equivalent circuit of Op-Amp ii) transfer characteristics of Op-Amp. (8)

MODULE II

13. a) Explain the working of an inverting comparator with necessary waveforms. (5)
- b) Describe the working of an instrumentation amplifier using Op-Amp and transducer bridge. (9)

OR

14. a) Explain the working of a temperature compensated logarithmic amplifier. (7)
- b) Explain the working of practical differentiator with necessary diagrams and analyze its frequency response. (7)

MODULE III

15. a) State the Bark-Hausen criteria for oscillation. Derive the frequency of oscillation for an RC phase shift Oscillator. (8)
- b) Design an astable multivibrator which produce square wave of frequency 2 KHz and V_{P-P} of 10V. (6)

OR

16. a) Explain how free running square waveform can be generated using Op-Amp. (7)
- b) Derive the transfer function of a second order high pass filter. (7)

MODULE IV

17. a) Explain the working of a monostable multivibrator using 555 timer IC with relevant waveforms and functional diagram. Derive an expression for the pulse width. (10)
- b) Describe how frequency multiplication can be achieved using a PLL. (4)

OR

18. a) Explain the working of an astable multivibrator using 555 timer IC with relevant waveforms and functional diagram. Derive the expression for frequency of oscillations. (10)
- b) Illustrate the principle of operation of a PLL with suitable diagrams. (4)

MODULE V

19. a) Describe the working of a current foldback protection circuit in regulators. (6)
- b) Explain the working of a R-2R ladder D/A converter. (8)

OR

20. a) Explain the working of low voltage regulator using IC723. (7)
- b) Illustrate the operation of dual slope ADC with a functional diagram. (7)
