

G 1569

(Pages : 2)

Reg. No.....

Name.....

**B.TECH. DEGREE EXAMINATION, MAY 2016**

**Fourth Semester**

Branch : Electrical and Electronics Engineering

EE 010 405 – DIGITAL SYSTEMS AND COMPUTER ORGANISATION [EE]

(New Scheme – 2010 Admission onwards)

[Regular/Improvement/Supplementary]

Time : Three Hours

Maximum : 100 Marks

**Part A**

*Answer all questions.*

*Each question carries 3 marks.*

1. Explain a combinational circuit.
2. What is a flip-flop?
3. Discuss the advantages of synchronous counters.
4. What is an Instruction cycle?
5. What is PCL?



(5 × 3 = 15 marks)

**Part B**

*Answer all questions.*

*Each question carries 5 marks.*

6. State and explain De-Morgan's Theorem.
7. Explain Sequential Circuits.
8. Draw a ring counter and explain its operation.
9. Explain Carry Look Ahead Adder and discuss its advantages.
10. Illustrate the advantages of a Dynamic RAM.

(5 × 5 = 25 marks)

**Part C**

*Answer all questions.*

*Each full question carries 12 marks.*

11. (a) Explain 8 : 1 MUX with a neat schematic diagram.  
(b) Draw a BCD to 7 segment decoder.

(6 + 6 = 12 marks)

Or

Turn over

12. (a) Explain CMOS, NAND and NOR gate.  
(b) Discuss the characteristic features of CMOS logic family.

(6 + 6 = 12 marks)

13. (a) What is Race around condition? How is it avoided?  
(b) Explain the operation of Master Slave JK Flip-flop using gates with a neat figure.

(3 + 9 = 12 marks)

Or

14. Design a Mod 12 Ripple Counter and explain.  
15. Design a Mod 7 synchronous counter.

Or

16. Explain the operation of the different types of Shift Registers.  
17. Explain the Processor Bus Structure.

Or

18. Explain Full Subtractor circuit with a block diagram. Design Full Subtraction circuit using basic gates.  
19. (a) Explain the Memory Hierarchy.  
(b) Write technical notes on the internal organisation of ROM.

(6 + 6 = 12 marks)

Or

20. (a) What are Buses?  
(b) Explain the standard IO interfaces briefly.

(3 + 9 = 12 marks)

[5 × 12 = 60 marks]

